

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned}$$


- ① In class, we derived the desired characteristics of an amplifier using the Y-parameter 2-port network.

$$\begin{aligned} I_1 &= Y_{11} V_1 + Y_{12} V_2 \\ I_2 &= Y_{21} V_1 + Y_{22} V_2 \end{aligned} \quad \text{where } Y = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$$

We saw that $\begin{bmatrix} 0 & 0 \\ Y_{21} & 0 \end{bmatrix}$ gives the best amplifier performance

Please repeat the same with H-parameters.

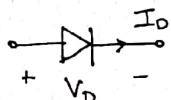
- ② The I-V characteristics of the diode is given by the equation:-



$$I_D = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$$

Derive its small signal equivalent.
 V_T is the thermal voltage (kT/q) and is 25mV at room temperature.

②

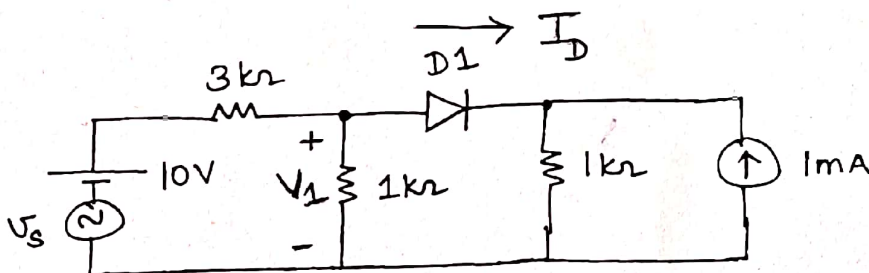

The diode D_1 has a forward voltage drop (built-in voltage) of 0.7V.

- (a) Assume $v_s = 0$. Calculate the current through the diode I_D .
 (b) Let v_s be a "small" input signal. Calculate the total voltage (dc + small signal) v_1 , when $v_s = 10\text{mV}$.