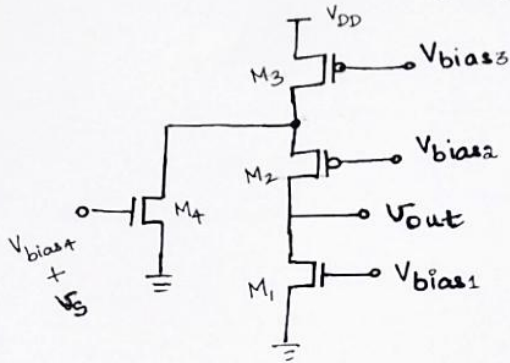


① Calculate the voltage gain of the following amplifier



$$\frac{V_{out}}{V_s} = ?$$

Note :- Assume $g_{mx} r_{dex} \gg 1$ for all x

② Calculate the voltage gain of the following amplifiers (V_o/V_s)

